

Exp.3A: Single-switch with low-side drive for DC motor.

Tasks

1

Build the drive and feedback circuit.

2

Read the datasheets of IR2110, ILD74, IL300, MCP601, IRF540, and 1N4007.


3

Justify the selection of the parameters in both circuits.


4




After learning code generation, test both circuits with a 24V Dcmotor.

Drive Circuit

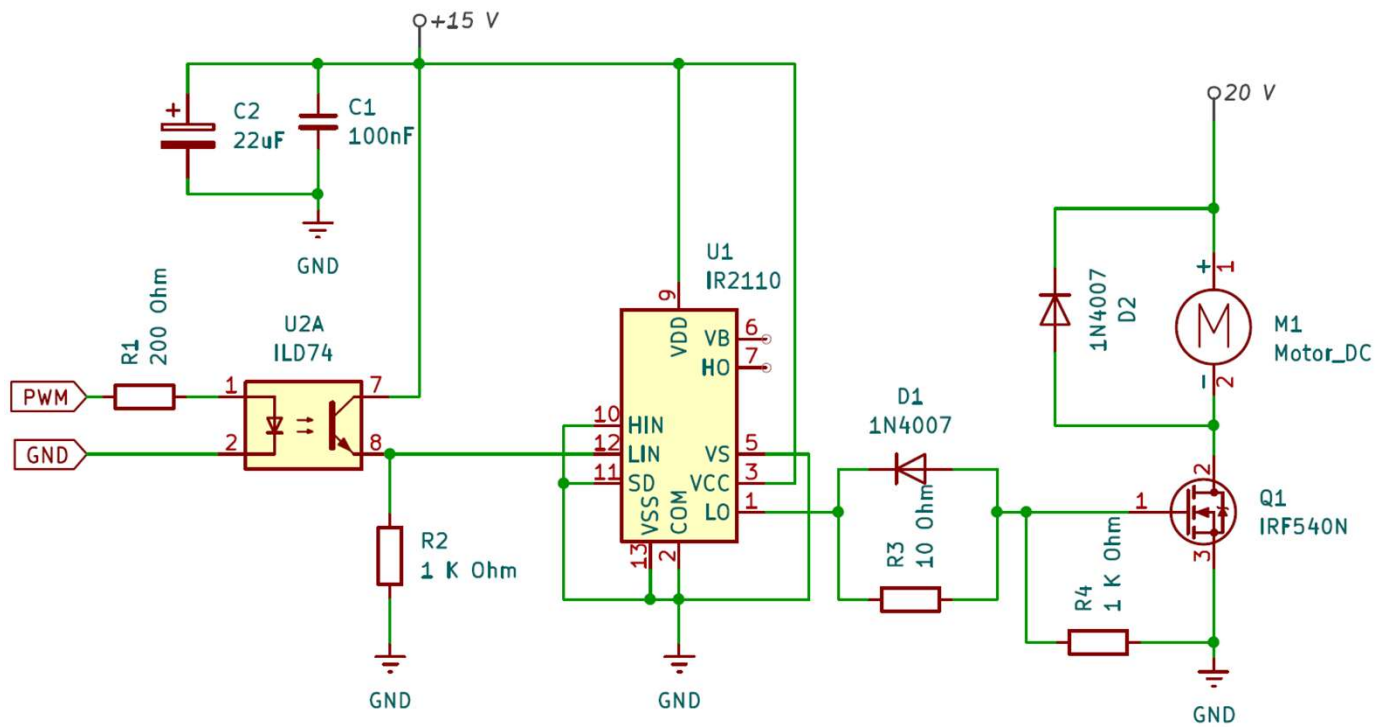

Feedback Circuit

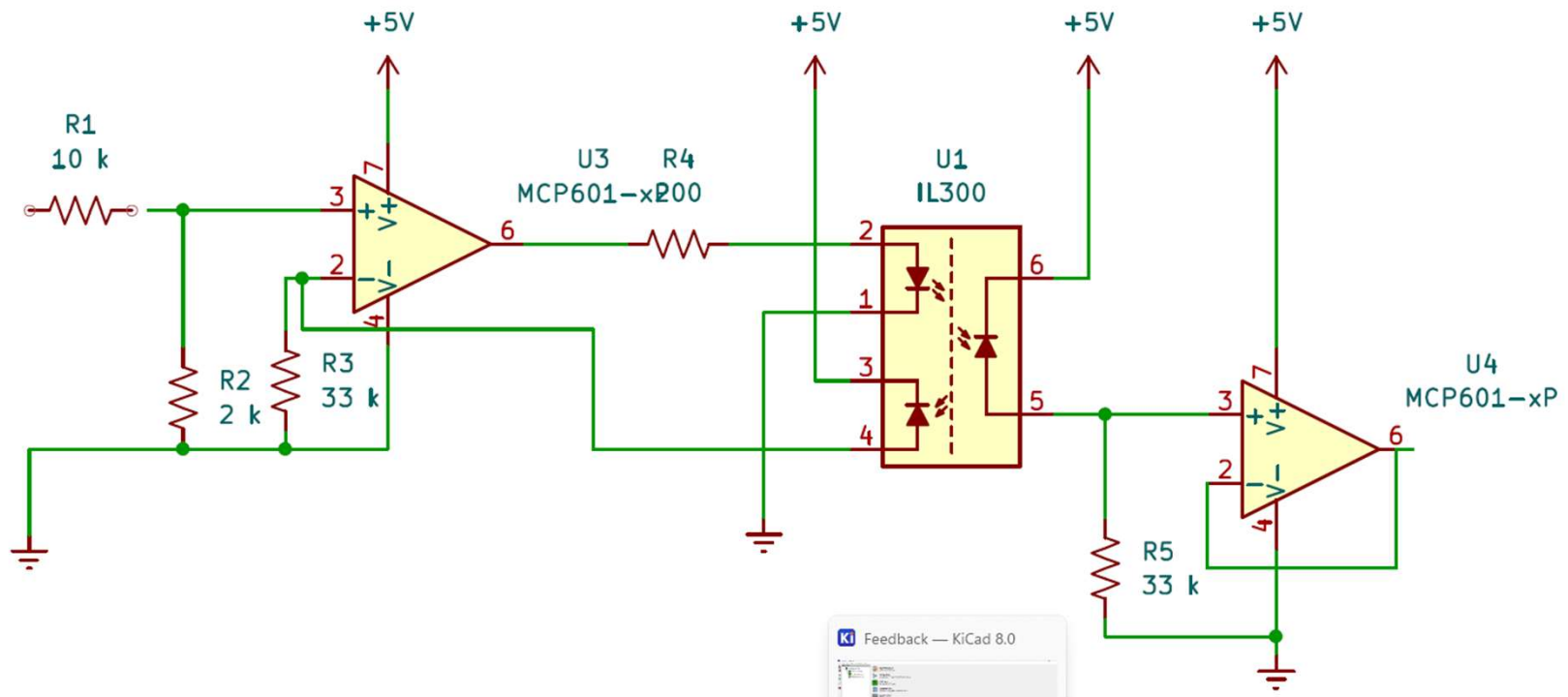

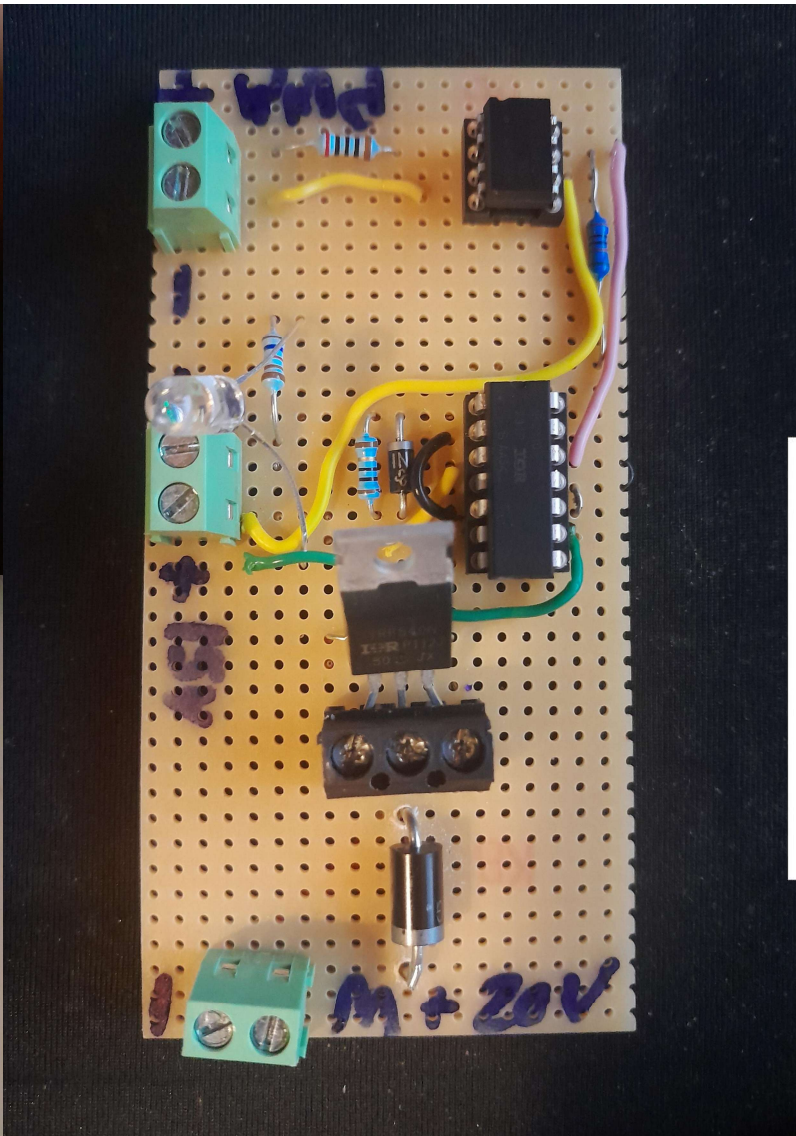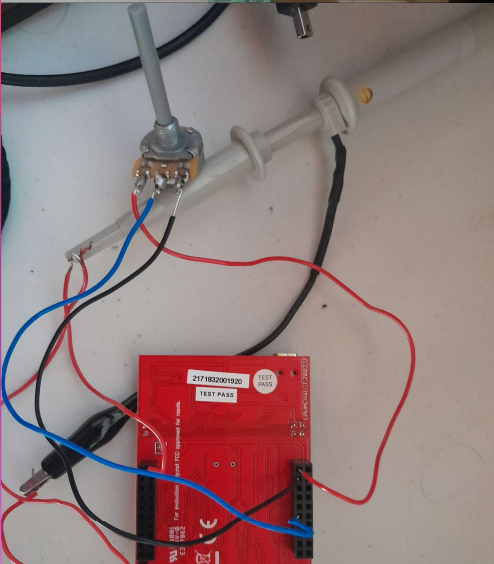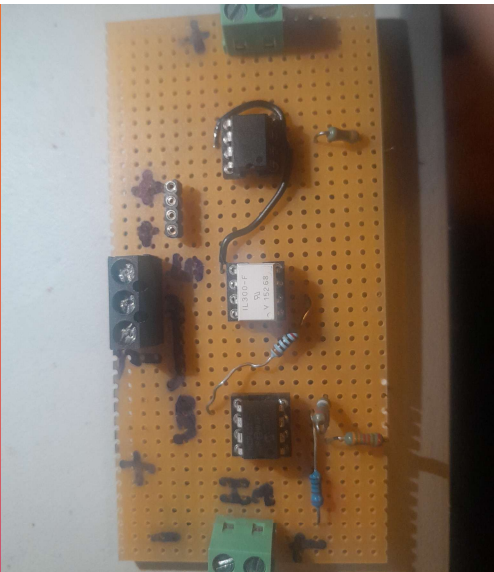

Implementation

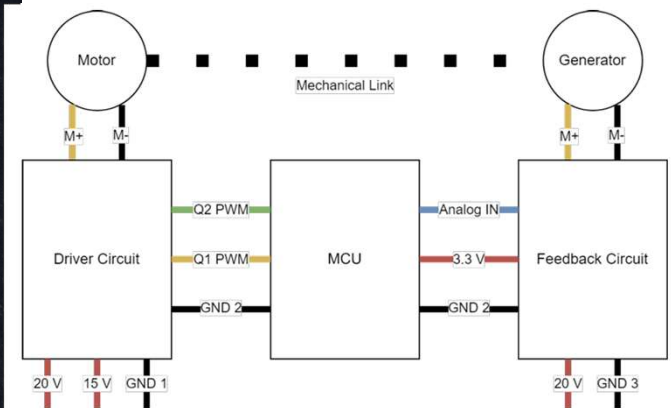


Figure 8: Block diagram of the system not including the optical sensor circuit

